

CAPACITOR SWITCHING DEVICE

Zero-Crossing Breaker

VS

Pre-Insertion Resistor

CAPACITOR SWITCHING DEVICE

Zero-Crossing Breaker

VS

Pre-Insertion Resistor

1. Method of Transient Control :

- 1.1. Zero-Crossing Breaker
- 1.2. Pre-Insertion Resistor

2. Design & Reliability :

- 2.1. Zero-Crossing Breaker vs Pre-Insertion Resistor

3. Computer Simulation of Capacitor Switching Transients :


- 3.1. Zero-Crossing Breaker vs Pre-Insertion Resistor
- 3.2. Summary & Conclusion
- 3.3. Reference :
"Pre-Insertion Resistors in HV Capacitor Bank Switching"

Method of Transient Control

1.1. Zero-Crossing Breaker

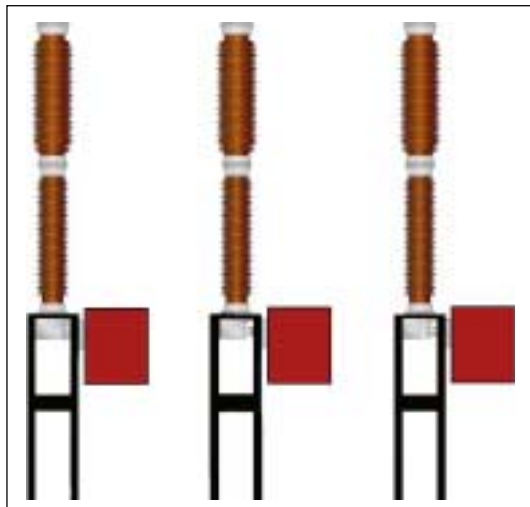1.2. Pre-Insertion Resistor


Method of Transient Control Zero-Crossing Breaker



+




Synchronous Closing Device

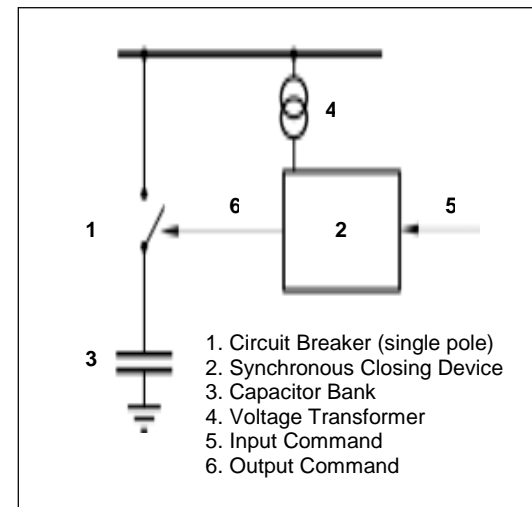


THREE "MUST" CONDITIONS :

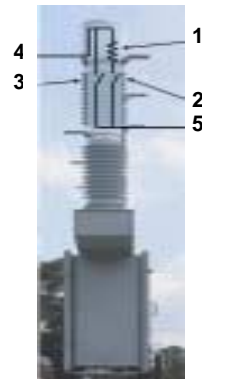1. CLOSING of ALL 3 PHASES at a ZERO VOLTAGE is a MUST
2. PRECISE TUNING and CONTROL of the 3 INDIVIDUAL POLES is a MUST
3. NO DRIFT of TIMING CALIBRATION is a MUST

Method of Transient Control Pre-Insertion Resistor



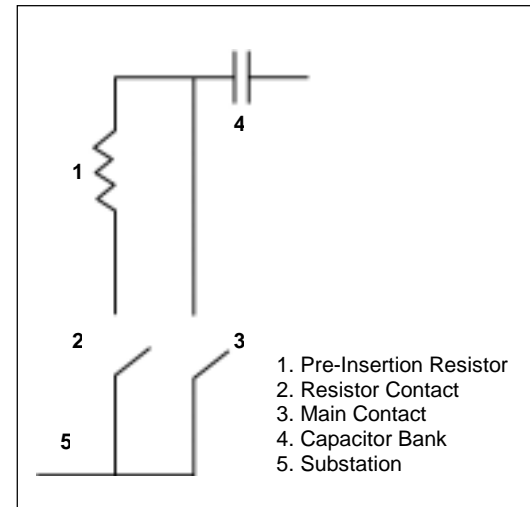1. Pre-Insertion Resistor
2. Resistor Contact
3. Main Contact
4. Capacitor Bank
5. Substation



“RESISTORS” (1) are typically inserted into the capacitive-energizing circuit through the closing of “RESISTOR CONTACT” (2) for 5 ms to 15 ms, prior to the closing of the “MAIN CONTACT” (3).

Design & Reliability

2.1. Zero-Crossing Breaker vs Pre-Insertion Resistor

Design & Reliability

Zero-Crossing Breaker vs Pre-Insertion Resistor

2.1

Description		ZERO-CROSSING BREAKER	PRE-INSERTION RESISTOR
1.	Specifically Designed and Tested for Capacitor Switching	No	Yes
2.	Number of Operating Mechanisms (spring loaded systems, shunt trips, motor operators)	3 (one per phase)	1 (one for 3 phases)
3.	Allows Two or One Phase Closing of the Capacitor Bank (if one operating mechanism fails to operate)	Yes	No
4.	Key Factor for Successful Transient Suppression	<ul style="list-style-type: none"> • Capacitor Bank must be switched exactly when the voltage is crossing ZERO. • Electronic circuitry must successfully detect when the voltage wave is crossing ZERO and order the mechanical mechanism that drives the interrupter to close. • Complicated calculation are required to offset effects of external conditions, mechanical wear, etc. 	<ul style="list-style-type: none"> • Simple electrical principle of a resistor in the circuit. • Key factor is simple physics.
5.	Reliability Factors	<ul style="list-style-type: none"> • Synchronous closing system is hard to maintain within required precision. • A highly precise electronic system tied to a mechanical device (interrupter) is not a guarantee for performance. 	<ul style="list-style-type: none"> • Highly reliable

Computer Simulation of Capacitor Switching Transients

**3.1. Zero-Crossing Breaker vs
Pre-Insertion Resistor**


3.2. Summary & Conclusion

**3.3. Reference :
“Pre-Insertion Resistors in
HV Capacitor Bank Switching”**

Computer Simulation of Capacitor Switching Transients


3.1

Zero-Crossing Breaker

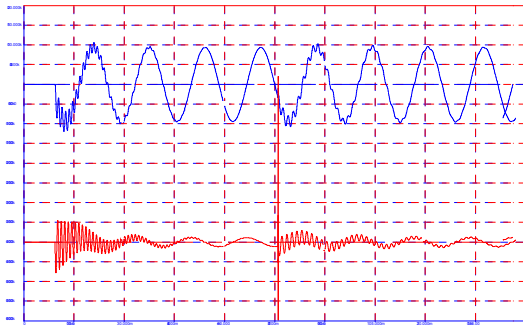

Voltage and Current for Energization of 1st Bank


Zero-crossing Breaker	Peak Current	Frequency	Peak Voltage
Bank 1 Energization	942A	944Hz	120kV (1.28pu)
Bank 2 Transient	5021A	16,807Hz	108kV (1.15pu)
Bank 2 Ringing	419A	672Hz	

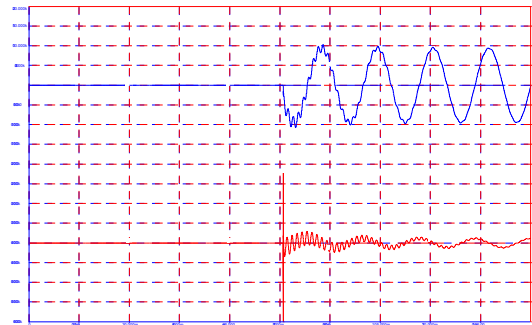

Voltage and Current for Energization of 2nd Bank


Zero-crossing Breaker	Peak Current	Frequency	Peak Voltage
Bank 2 Energization	5228A	16,667Hz	108kV (1.15pu)
Bank 2 Ringing	420A	670Hz	

Pre-Insertion Resistor

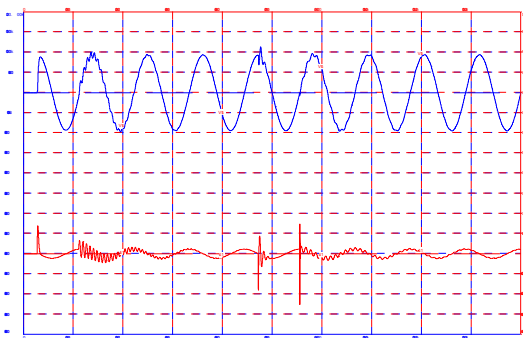

Voltage and Current for Energization of 1st Bank at 80 Ohms

Pre-insertion Resistor	Peak Current	Frequency	Peak Voltage
Bank 1 Energization	835A	NA	97kV (1.03pu)
Bank 1 Transient	404A	948Hz	101kV (1.07pu)
Bank 2 Energization	1100A	809Hz	114kV (1.21pu)
Bank 2 Transient	1520A	16,400Hz	
Bank 2 Ringing	235A	670Hz	97kV (1.03pu)

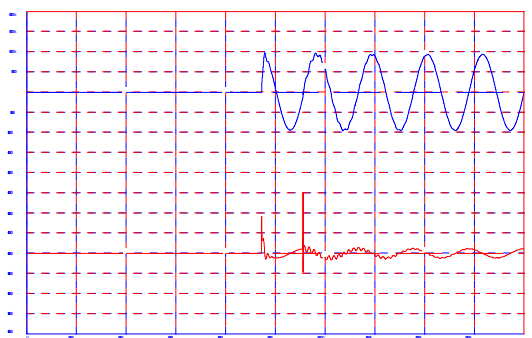

Voltage and Current for Energization of 2nd Bank at 80 Ohms

Pre-insertion Resistor	Peak Current	Frequency	Peak Voltage
Bank 2 Energization	1100A	892Hz	98.7kV (1.05pu)
Bank 2 Transient	1820A	16,529Hz	
Bank 2 Ringing	235A	672Hz	98.3kV (1.05pu)

In addition, the I^2t for the 80 ohm pre-insertion resistor is $330A^2s$.

Computer Simulation of Capacitor Switching Transients

3.2

Summary

Simulation Case	Single-Bank		Back-to-Back		PEAK VOLTAGE
	PEAK CURRENT	FREQUENCY	PEAK CURRENT	FREQUENCY	
ZERO-CROSSING BREAKER (1 ms error)	942 A	944 Hz	5021 A	16.807 Hz	1.28 pu
PRE-INSERTION RESISTOR (80Ω)	835 A	948 Hz	1820 A	16.529 Hz	1.22 pu

Remarks : All above values are summarized from the most significant data.

Conclusion

Simulation Case	Mitigation of CURRENT TRANSIENTS	Mitigation of VOLTAGE TRANSIENTS	Remarks
ZERO-CROSSING BREAKER (1 ms error)	Successful	Good	TRANSIENTS will INCREASE, if "TIMING CALIBRATION" DRIFTS
PRE-INSERTION RESISTOR (80 Ω)	Successful	Significant	

"Pre-Insertion Resistor in
HV Capacitor Bank Switching"

Prepared for :
Western Protective Relay Conference
October 19 - 21, 2004
Spokane, WA